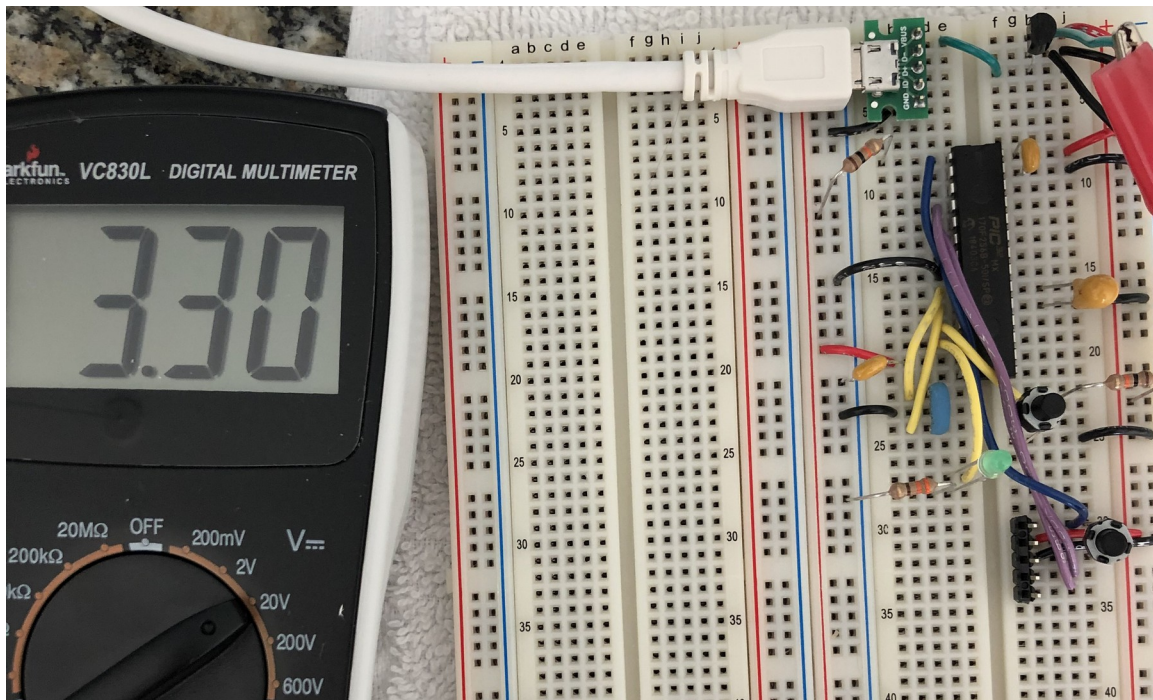



Homework #1

I currently don't have an nScope, so I took pictures of the multimeter output for the build/test voltage regulator section.


- Regulator output voltage, no bypass capacitors/LED



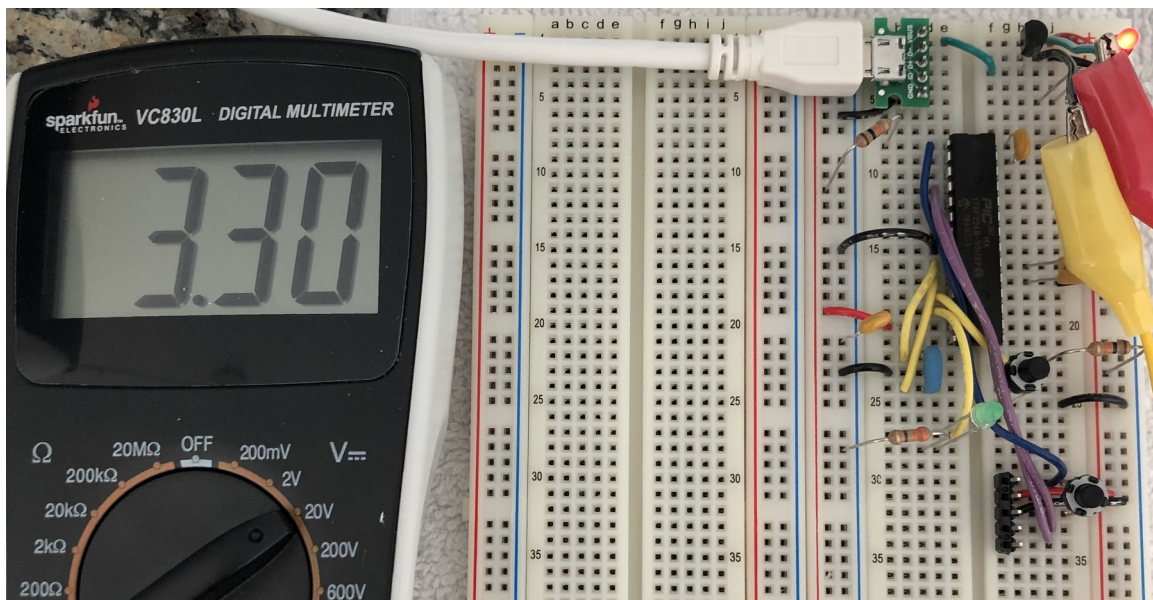
- Regulator output voltage including red LED, no bypass capacitors



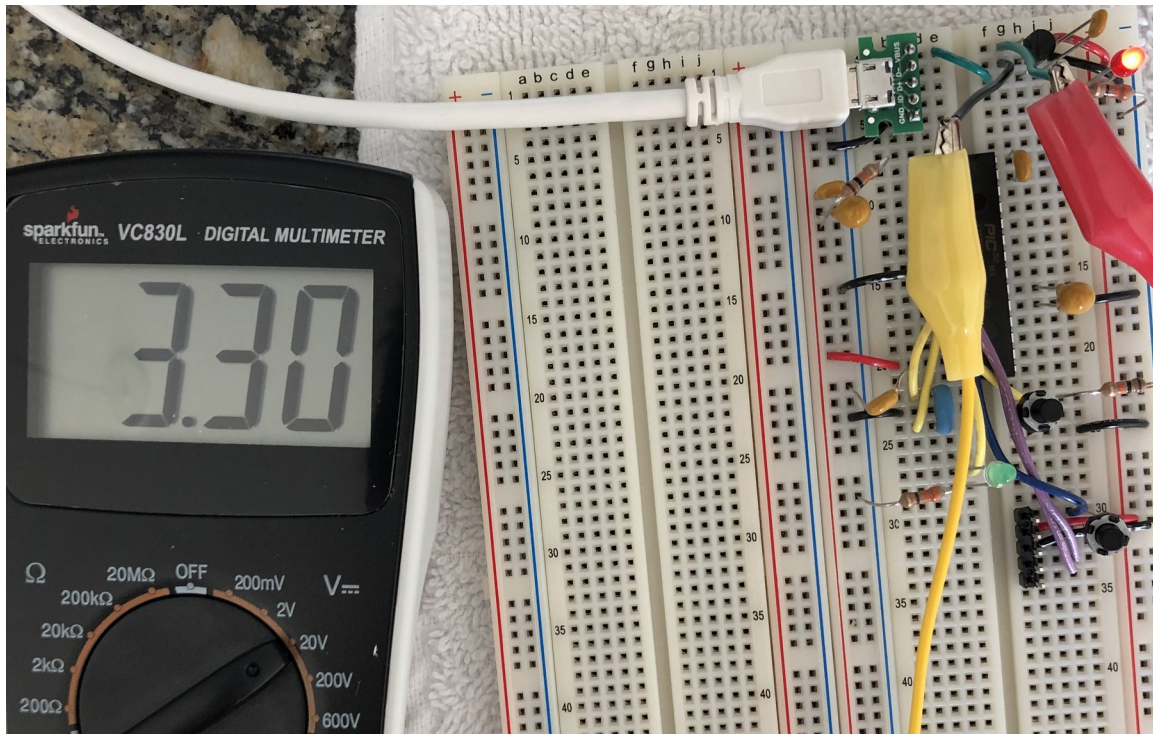- Regulator output voltage, including red LED and bypass capacitors



- Circuit diagram

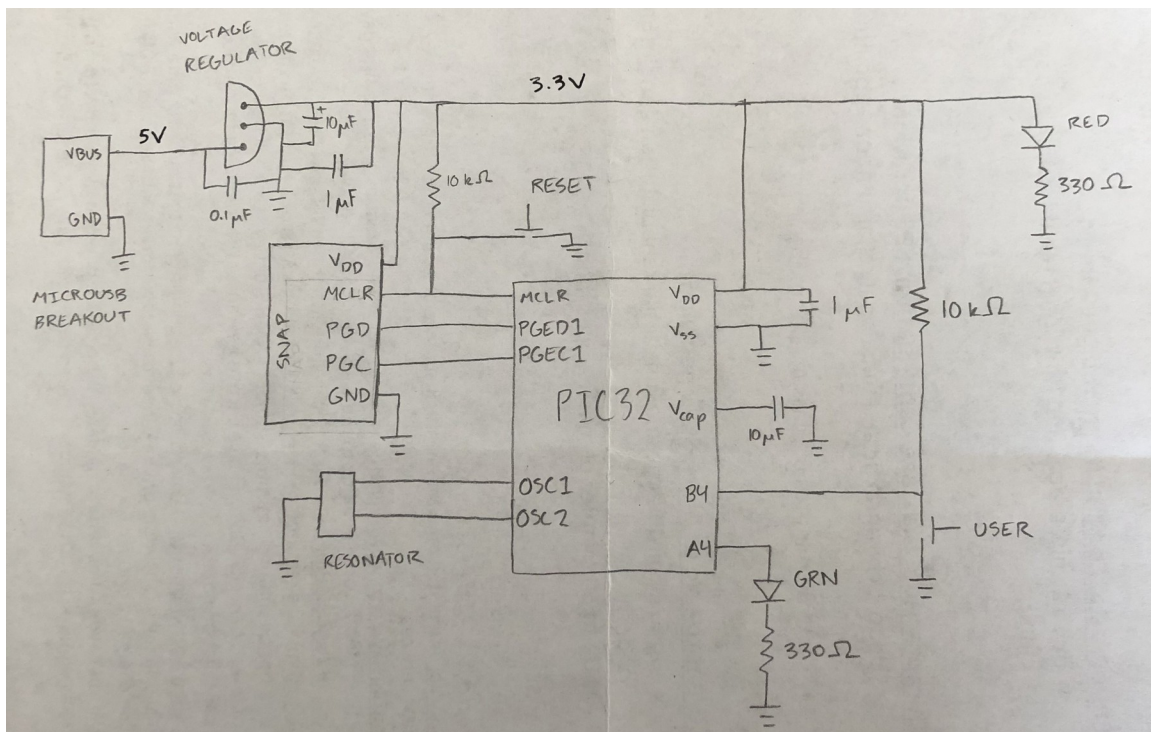

- Physical circuit

